

# EXPERIMENT NO : 1

## Aim of the Experiment :

Analysis of small signal BJT Amplifier using eSim.


## Theory :

In the Bipolar Transistor the most common circuit configuration for an NPN transistor is that of the **Common Emitter Amplifier** circuit and that a family of curves known commonly as the **Output Characteristic Curves**, relate the transistors Collector current ( $I_c$ ), to the Collector voltage ( $V_{ce}$ ) for different values of Base current ( $I_b$ ).

All types of Transistor Amplifiers operate using AC signal inputs which alternate between a positive value and a negative value so some way of “presetting” the amplifier circuit to operate between these two maximum or peak values is required. This is achieved using a process known as Biasing. Biasing is very important in amplifier design as it establishes the correct operating point of the transistor amplifier ready to receive signals, thereby reducing any distortion to the output signal.

The DC load line can be drawn onto these output characteristics curves to show all the possible operating points of the transistor from fully “ON” to fully “OFF”, and to which the quiescent operating point or **Q-point** of the amplifier can be found. The aim of any small signal amplifier is to amplify all of the input signal with the minimum amount of distortion possible to the output signal, in other words, the output signal must be an exact reproduction of the input signal but only bigger (amplified).

To obtain low distortion when used as an amplifier the operating quiescent point needs to be correctly selected. This is in fact the DC operating point of the amplifier and its position may be established at any point along the load line by a suitable biasing arrangement. The best possible position for this Q-point is as close to the center position of the load line as reasonably possible, thereby producing a Class A type amplifier operation, ie.  $V_{ce} = 1/2V_{cc}$ . Consider the Common Emitter Amplifier circuit shown below.

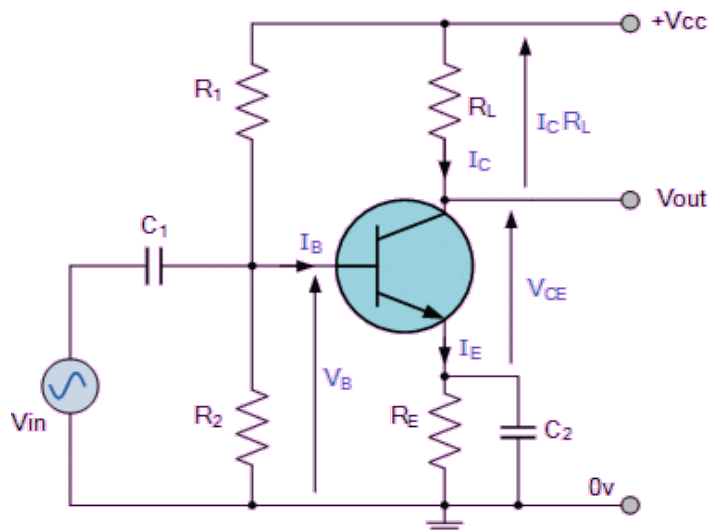

The single stage common emitter amplifier circuit shown above uses what is commonly called “Voltage Divider Biasing”. This type of biasing arrangement uses two resistors as a potential divider network across the supply with their center point supplying the required Base bias voltage to the transistor. Voltage divider biasing is commonly used in the design of bipolar transistor amplifier circuits. This method of biasing the transistor greatly reduces the effects of varying Beta, ( $\beta$ ) by holding the Base bias at a constant steady voltage level allowing for best stability. The quiescent Base voltage ( $V_b$ ) is determined by the potential divider network formed by the two resistors,  $R_1$ ,  $R_2$  and the power supply voltage  $V_{cc}$ .

Then the total resistance will be equal to  $R_1 + R_2$  giving the current as  $i = V_{cc}/R_1+R_2$ . The voltage level generated at the junction of resistors  $R_1$  and  $R_2$  holds the Base voltage ( $V_b$ ) constant at a value below the supply voltage.


Then the potential divider network used in the common emitter amplifier circuit divides the input signal in proportion to the resistance. This bias reference voltage can be easily calculated using the simple voltage divider formula below:

**Bias voltage**


$$V_b = V_{cc} \frac{R_2}{R_1+R_2}$$

Beta has no units as it is a fixed ratio of the two currents,  $I_c$  and  $I_b$  so a small change in the Base current will cause a large change in the Collector current. As the Base/Emitter junction is forward-biased, the Emitter voltage,  $V_e$  will be one junction voltage drop different to the Base voltage. If the voltage across the Emitter resistor is known then the Emitter current,  $I_e$  can be easily calculated using **Ohm’s Law**. The Collector current,  $I_c$  can be approximated, since it is almost the same value as the Emitter current.


**Schematic diagram:**

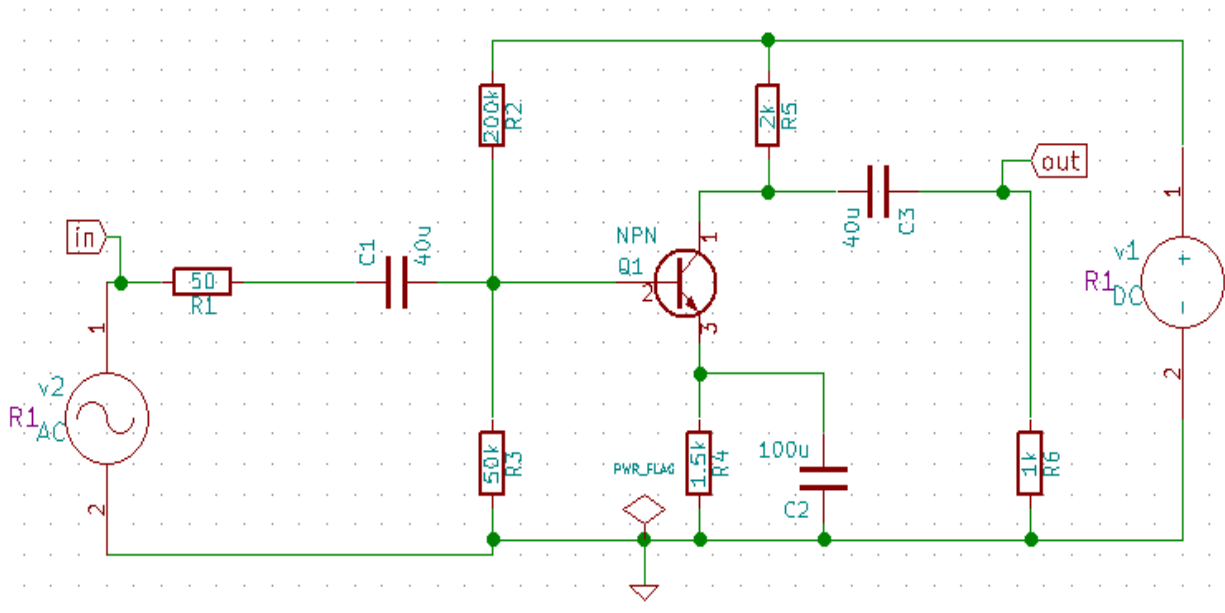

## Waveform:

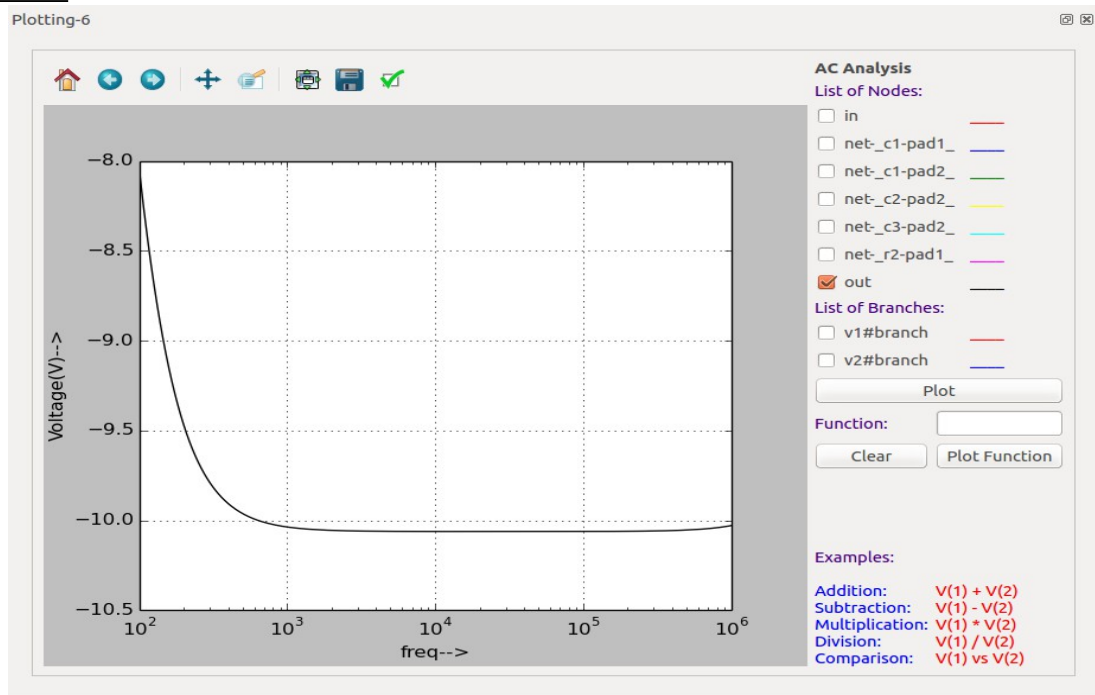

## Python plot output

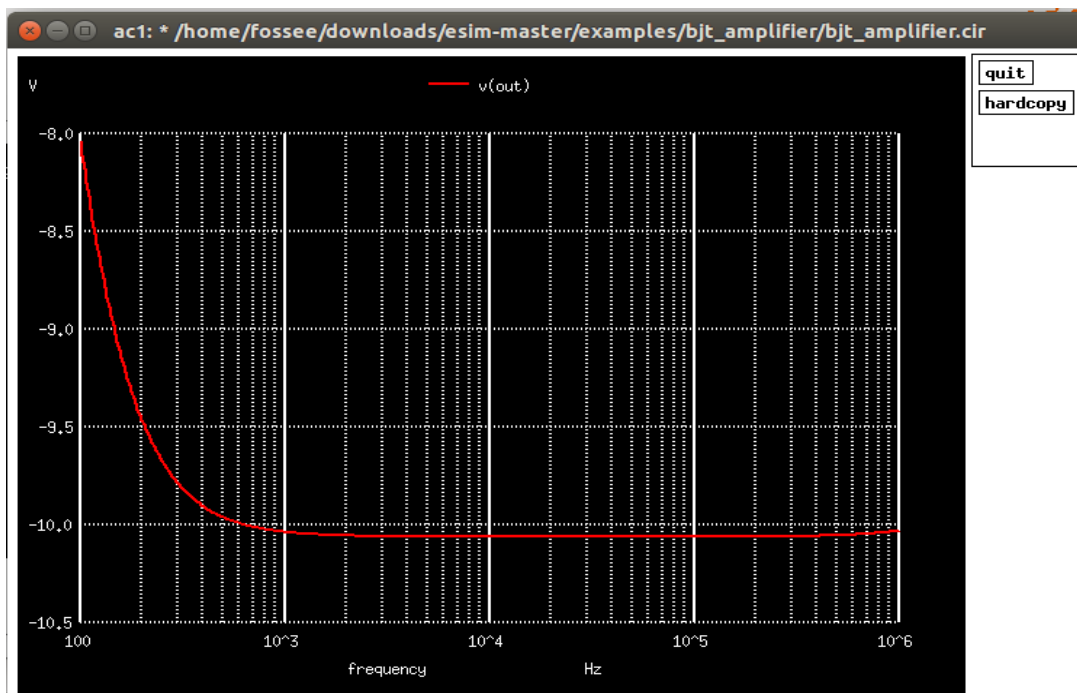

## Ngspice plot output

## Conclusion :

Thus we have studied the BJT amplifier using eSim and we get the appropriate waveforms.

## References :

<http://www.electronics-tutorials.ws>